

(Exchange circuit analysis by VD4)

20/Dec. 2003 Ver 1.0



Electro Systems Engineering

ESE SERVICE



..... Table of contents

1 The purpose of VD4 development

1-1 The present condition of functional grasp of electric equipment

1-2 The necessity for VD4

1-3 Copyright registration

2 Composition of impedance

$$\left(\dot{Z}\right)^n = \left(\dot{Z}_1\right)^n + \left(\dot{Z}_2\right)^n$$

2-1 Series circuit $n = 1$

2-2 Parallel circuit $n = -1$

2-3 The error by simple calculation of a series circuit

$$\varepsilon = (1/\cos \phi) - 1$$

3 The circuit diagram for calculation

3-1 The circuit diagram

3-2 Calculation procedure

3-3 Calculation by impedance composition

4 Calculation by VD4

4-1 VD4 Work sheet

4-2 VD4 Data sheet

5 Electric apparatus load list

5-1 Electric apparatus load list summary sheet

5-2 Electric apparatus load list

5-3 Electric apparatus load list data sheet

6 Exchange circuit analysis by VD4

6-1 Short-circuit current calculation

6-2 About a power factor improvement

6-3 About a series reactor

6-4 Reliability of load list

7 The plan of electric equipment

7-1 Master plan

7-2 Enforcement plan

8 Maintenance management of electric equipment

8-1 Various imitation construction

8-2 Various diagnostic tests

8-3 Karte [Data base] registration



1 The purpose of VD4 development

1-1 The present condition of functional grasp of electric equipment

Grasping correctly the function (electric power supply capability, the margin of apparatus and wiring, maintenance of proper voltage, influence by instant voltage descent, power factor adjustment) of electric equipment -- the plan of this electric equipment, construction, and maintenance management -- in any case, it is important.

This is indispensable to correspondence to the safety of electric equipment, economical efficiency, and load change.

However, the equipment of the present condition of electric equipment is not proper to load, or it has some which have not performed maintenance of proper voltage.

1-2 The necessity for VD4

Exchange circuit analysis is needed as a means of functional grasp of electric equipment.

Therefore, the special feature of change of incoming voltage, the capacity of a power transformer, the existence of an electric power capacitor, an electric system, the wiring method, and the load to change etc. must be examined, and the power distribution network which results in each load must be analyzed as one system after electric equipment.

The impedance composition calculation by **the Ohm method** was adopted as this means, and the voltage value and current value in each part grade, power factor, the rate of transformer load, transformer voltage rate of change, the short-circuit current, etc. were calculated correctly.

While the feature of the analysis by this **Ohm method** is easy work which depends even a formula ($E=IZ$), the complicated work of impedance composition is accompanied by it.

For this reason, it is clear in manual calculation that it is not practical.

Then, calculation processing in the minimum input time and effort and a short time was realizable using "Excel" of U.S. Microsoft Corp. with the high present flexibility.

1-3 Copyright registration


In case A.D. 2000 came around, in accordance with **VD2** (high-voltage circuit analysis) and **VD3** (induction motor circuit analysis), copyright registration of this exchange circuit analysis VD4 was carried out.

Although **VD** of **VD** series is the pet name attached from the initial of Voltage drop, it does not stop only at calculation of track voltage drop, but expects continuing developing into the diversity covering an exchange circuit at large as surprising calculation software for business.

registration number **P the 6556th** -- No.1 November 26, 1999 **Software Information Center**, Japan

2 Composition of impedance

2-1 Series circuit

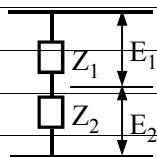

When synthetic impedance is set to Z , it is from $E = IZ$ and $E = E_1 + E_2$

Since it is $IZ = E_1 + E_2 = IZ_1 + IZ_2$, synthetic impedance is set to $\dot{Z} = \dot{Z}_1 + \dot{Z}_2$

$$Z = (R_1 + R_2) + j(X_1 + X_2) \quad \text{at } Z_1 = R_1 + jX_1, Z_2 = R_2 + jX_2 \quad F-11$$


$$Z = R_1 + j\{X_1 - (1/X_c)\} \quad \text{at } Z_1 = R_1 + jX_1, Z_2 = 1/jX_c \quad F-12$$

Here, $X = \omega L = 2\pi fL$, $X_c = \omega C = 2\pi fC$

$$\cos\phi = (R_1 + R_2)/Z \quad F-13$$

$$\cos\phi = R_1/Z \quad F-14$$

2-2 Parallel circuit

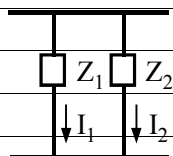

When synthetic impedance is set to Z , it is from $E = IZ$ and $I = I_1 + I_2$

Since it is $IZ = (I_1 + I_2)Z$, $I_1 = E/Z_1$, $I_2 = E/Z_2$, $E = \{(E/Z_1) + (E/Z_2)\}Z$

synthetic impedance is set to $\left(\frac{1}{Z}\right) = \left(\frac{1}{Z_1}\right) + \left(\frac{1}{Z_2}\right)$ or $\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2}$

at $Z_1 = R_1 + jX_1$, $Z_2 = R_2 + jX_2$

$$\frac{1}{Z} = \left(\frac{R_1}{R_1^2 + X_1^2} + \frac{R_2}{R_2^2 + X_2^2} \right) - j \left(\frac{X_1}{R_1^2 + X_1^2} + \frac{X_2}{R_2^2 + X_2^2} \right) \quad F-21$$

$$Z = \frac{R_1(R_2^2 + X_2^2) + R_2(R_1^2 + X_1^2)}{(R_1 + R_2)^2 + (X_1 + X_2)^2} + j \frac{X_1(R_2^2 + X_2^2) + X_2(R_1^2 + X_1^2)}{(R_1 + R_2)^2 + (X_1 + X_2)^2} \quad F-22$$

at $Z_1 = R_1 + jX_1$, $Z_2 = 1/jX_c$

$$\frac{1}{Z} = \left(\frac{R_1}{R_1^2 + X_1^2} \right) - j \left(\frac{X_1}{R_1^2 + X_1^2} + \frac{1}{X_c} \right) \quad F-23$$

$$Z = \frac{R_1}{(R_1 X_c)^2 + (X_c X_1 - 1)^2} + j \frac{X_1 - X_c(R_1^2 + X_1^2)}{(R_1 X_c)^2 + (X_1 X_c - 1)^2} \quad F-24$$

Here, $X = \omega L = 2\pi fL$, $X_c = \omega C = 2\pi fC$

$$\cos\phi = [\{R_1(R_2^2 + X_2^2) + R_2(R_1^2 + X_1^2)\} / \{(R_1 + R_2)^2 + (X_1 + X_2)^2\}] / Z \quad F-25$$

$$\cos\phi = [R_1 / \{(R_1 X_c)^2 + (X_c X_1 - 1)^2\}] / Z \quad F-26$$

2-3 The error by simple calculation of a series circuit

The error ϵ when carrying out simple calculation of the $\dot{Z} = \dot{Z}_1 + \dot{Z}_2$ as $Z = |Z_1| + |Z_2|$

serves as the following formula.


$$\epsilon = \dot{Z}_1 + \dot{Z}_2 - |Z_1| - |Z_2| = \sqrt{(R_1 + R_2)^2 + (X_1 + X_2)^2} - \sqrt{R_1^2 + X_1^2} - \sqrt{R_2^2 + X_2^2}$$

$\dot{Z}_1 + \dot{Z}_2 \leq |Z_1| + |Z_2|$ is realized here.

Although an error is not produced only when all of $\cos\phi$ of Z , Z_1 , and Z_2 are the same values by the upper formula, when that is not right, a simple calculation value becomes actually more large.

To Z when $\cos\phi$ of Z_1, Z_2 is ± 0.95 , the error is set to $+5.26\%$

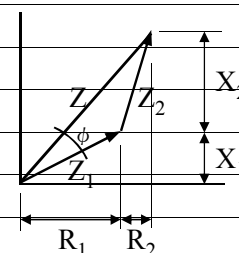To Z when $\cos\phi$ of Z_1, Z_2 is ± 0.85 , the error is set to $+17.64\%$




3 The circuit diagram for calculation

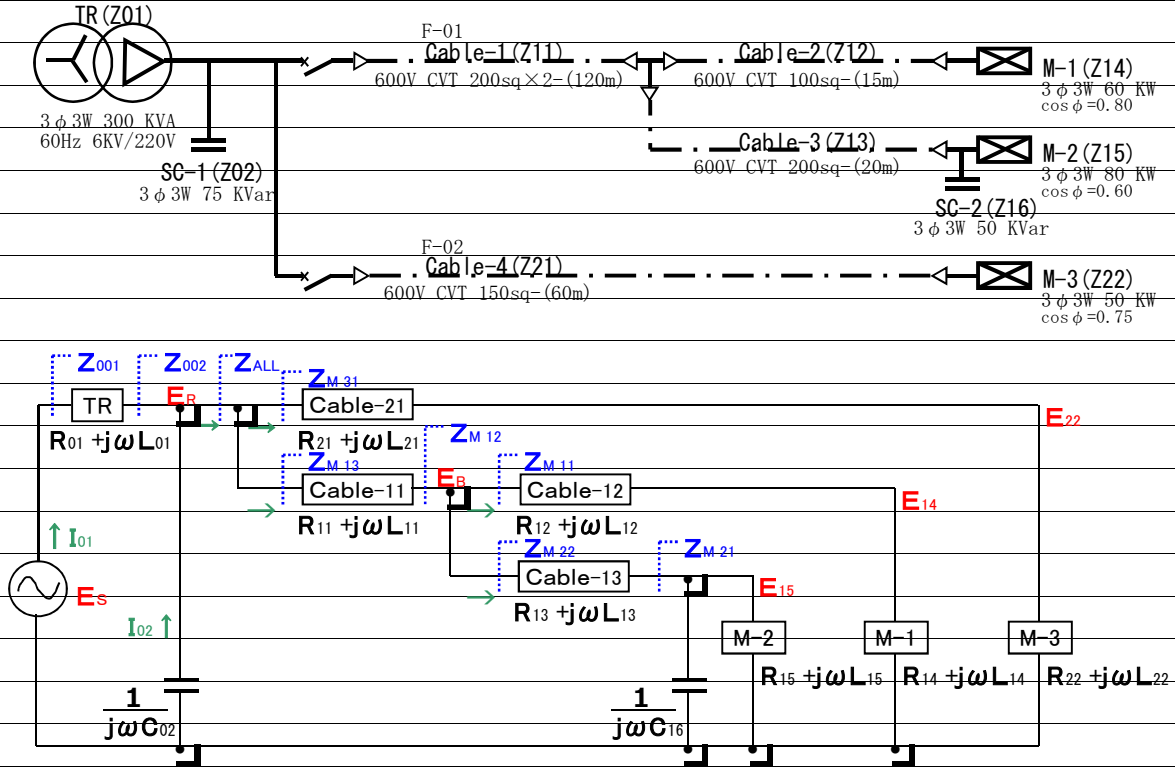3-1 The circuit diagram

The following circuit is assumed in order to check the calculation value of the exchange circuit analysis by VDA.

Calculation temperature is set to 50 [°C].



3-2 Calculation procedure [] An inside sign expresses the impedance composition formula of a front page.

Impedance composition calculation

The current value, voltage value calculation

01 : $Z_{15}, Z_{16} \Rightarrow Z_{M21}$ [F-24]

11 : $I_{01} = E_S / Z_{001}$ (Transformer current)

02 : $Z_{M21}, Z_{13} \Rightarrow Z_{M22}$ [F-11]

12 : $E_R = I_{01} \times Z_{002}$ (Power distribution side voltage)

13 : $I_{ALL} = E_R / Z_{ALL}$ (All load current)

03 : $Z_{14}, Z_{12} \Rightarrow Z_{M11}$ [F-11]

14 : $I_{21} = E_R / Z_{M31}$ (Load current of M-3)

04 : $Z_{M11}, Z_{M22} \Rightarrow Z_{M12}$ [F-22]

15 : $E_{22} = I_{21} \times Z_{22}$ (Primary board side terminal voltage of M-3)

05 : $Z_{M12}, Z_{11} \Rightarrow Z_{M13}$ [F-11]

06 : $Z_{22}, Z_{21} \Rightarrow Z_{M31}$ [F-11]

16 : $I_{11} = E_R / Z_{M13}$ (Load current of M-1, -2)

07 : $Z_{M13}, Z_{M31} \Rightarrow Z_{ALL}$ [F-22]

17 : $E_B = I_{11} \times Z_{M12}$ (Branch part voltage)

18 : $I_{12} = E_B / Z_{M11}$ (Load current of M-1)

08 : $Z_{ALL}, Z_{02} \Rightarrow Z_{002}$ [F-24]

19 : $E_{14} = I_{12} \times Z_{14}$ (Primary board side terminal voltage of M-1)

09 : $Z_{002}, Z_{01} \Rightarrow Z_{001}$ [F-11]

20 : $I_{13} = E_B / Z_{M22}$ (Load current of M-2)

10 : $Z_{15}, Z_{16} \Rightarrow \cos \phi$ [F-26]

21 : $E_{15} = I_{13} \times Z_{M21}$ (Primary board side terminal voltage of M-2)

$\cos \phi$ is average power factor of M-2.

**3-3 Calculation by impedance composition****01 : Z_{15} , $Z_{16} \Rightarrow Z_{M21}$ [F-24]**KW= 80 $\cos \phi = 0.6000$ $E_s[V] = 220$ SC[KVA]= 50 The completion $Z_{15} = 80[KW] / \cos \phi = 80 \times 10^3 / = 133333.3 \text{ } [\Omega]$ $Z = E^2 / [KVA] = 0.363 \text{ } [\Omega]$ $R_{15} = \sqrt{3} \cdot Z \cdot \cos \phi = \sqrt{3} \cdot 0.363[\Omega] \cdot 0.6 = 0.377241 \text{ } [\Omega]$, $X_{14} = \sqrt{3} \cdot 0.363[\Omega] \sqrt{(1-0.6^2)} = 0.502988 \text{ } [\Omega]$ $Z_{16} : Z = E^2 / [KVar] = 220^2 / (50 \cdot 10^3) = 0.968000 \text{ } [\Omega]$, $1/X_{16} = \sqrt{3} \cdot 0.968 \rightarrow X_{16} = 0.596436 \text{ } [\Omega]$ If $Z_{M21} = R_{M21} + j X_{M21}$, $R_{15} = 0.377241$ $X_{15} = 0.502988$ $X_{16} = 0.596436$ $Z_{M21} = 0.697786 + j 0.494265 \text{ } [\Omega]$ **02 : Z_{M21} , $Z_{13} \Rightarrow Z_{M22}$ [F-11]** $R \text{ } [\Omega/Km] = 0.121$ $X \text{ } [\Omega/Km] = 0.0845$ al. temp. [°C]= 50 Cable span[m]= 20 The completion $Z_{13} : R_{13} = \sqrt{3} \cdot 0.121 \{1 + 0.00393 \cdot (50-20)\} / \{1 + 0.00393 \cdot (90-20)\} \cdot (20m/1000m) = 3.674808 \text{ } [m\Omega]$ $X_{13} = \sqrt{3} \cdot 0.0845 (60/50) \cdot (20m/1000m) = 3.512599 \text{ } [m\Omega]$ If $Z_{M22} = R_{M22} + j X_{M22}$, $R_{M21} = 0.697786$ $X_{M21} = 0.494265$ $R_{13} = 0.003675$ $X_{13} = 0.003513$ $Z_{M22} = 0.701461 + j 0.497778 \text{ } [\Omega]$ **03 : Z_{14} , $Z_{12} \Rightarrow Z_{M11}$ [F-11]**KW= 60 $\cos \phi = 0.8000$ $E_s[V] = 220$ The completion $Z_{14} = 60[KW] / \cos \phi = 60 \times 10^3 / = 75000 \text{ } [\Omega]$ $Z = E^2 / [KVA] = 0.645333 \text{ } [\Omega]$ $R_{14} = \sqrt{3} \cdot Z \cdot \cos \phi = \sqrt{3} \cdot 0.645[\Omega] \cdot 0.8 = 0.8942 \text{ } [\Omega]$, $X_{14} = \sqrt{3} \cdot 0.645[\Omega] \sqrt{(1-0.8^2)} = 0.67065 \text{ } [\Omega]$ $R \text{ } [\Omega/Km] = 0.24$ $X \text{ } [\Omega/Km] = 0.0883$ al. temp. [°C]= 50 Cable span[m]= 15 The completion $Z_{12} : R_{12} = \sqrt{3} \cdot 0.24 \{1 + 0.00393 \cdot (50-20)\} / \{1 + 0.00393 \cdot (90-20)\} \cdot (15m/1000m) = 5.466657 \text{ } [m\Omega]$ $X_{12} = \sqrt{3} \cdot 0.0883 (60/50) \cdot (15m/1000m) = 2.752922 \text{ } [m\Omega]$ If $Z_{M11} = R_{M11} + j X_{M11}$, $R_{14} = 0.8942$ $X_{14} = 0.67065$ $R_{12} = 0.005467$ $X_{12} = 0.002753$ $Z_{M11} = 0.899667 + j 0.673403 \text{ } [\Omega]$ **04 : Z_{M11} , $Z_{M22} \Rightarrow Z_{M12}$ [F-22]**If $Z_{M12} = R_{M12} + j X_{M12}$, $R_{M11} = 0.899667$ $X_{M11} = 0.673403$ $R_{M22} = 0.701461$ $X_{M22} = 0.497778$ $Z_{M12} = 0.394243 + j 0.286342 \text{ } [\Omega]$ **05 : Z_{M12} , $Z_{11} \Rightarrow Z_{M13}$ [F-11]** $R \text{ } [\Omega/Km] = 0.121$ $X \text{ } [\Omega/Km] = 0.0845$ al. temp. [°C]= 50 Cable span[m]= 120 The completion $Z_{11} : R_{13} = \sqrt{3} \cdot 0.121 \{1 + 0.00393 \cdot (50-20)\} / \{1 + 0.00393 \cdot (90-20)\} \cdot (120/1000) \cdot (1/2) = 11.02443 \text{ } [m\Omega]$ $X_{11} = \sqrt{3} \cdot 0.0845 (60/50) \cdot (120/1000) \cdot (1/2) = 10.5378 \text{ } [m\Omega]$ If $Z_{M13} = R_{M13} + j X_{M13}$, $R_{11} = 0.011024$ $X_{11} = 0.010538$ $R_{M12} = 0.394243$ $X_{M12} = 0.286342$ $Z_{M13} = 0.405268 + j 0.29688 \text{ } [\Omega]$



1

06 : Z_{22} , $Z_{21} \Rightarrow Z_{M31}$ [F-11]KW= 50 $\cos \phi = 0.7500$ $E_s[V] = 220$

The completion

 $Z_{22} = 50[KW] / \cos \phi = 50 \times 10^3 / = 66666.67 [\Omega]$ $Z = E^2 / [KVA] = 0.726 [\Omega]$ $R_{22} = \sqrt{3} \cdot Z \cdot \cos \phi = \sqrt{3} \cdot 0.726 [\Omega] \cdot 0.75 = 0.943102 [\Omega]$, $X_{22} = \sqrt{3} \cdot 0.726 [\Omega] \sqrt{(1-0.75^2)} = 0.831737 [\Omega]$ $R [\Omega/Km] = 0.159$ $X [\Omega/Km] = 0.0839$ al. temp. [°C]= 50 Cable span[m]= 60 The completion $Z_{21} : R_{21} = \sqrt{3} \cdot 0.159 \{1 + 0.00393 \cdot (50-20)\} / \{1 + 0.00393 \cdot (90-20)\} \cdot (60m/1000m) = 14.48664 [m\Omega]$ $X_{21} = \sqrt{3} \cdot 0.0839 (60/50) \cdot (60m/1000m) = 10.46297 [m\Omega]$ If $Z_{M31} = R_{M31} + jX_{M31}$, $R_{22} = 0.943102$ $X_{22} = 0.831737$ $R_{21} = 0.014487$ $X_{21} = 0.010463$ $Z_{M31} = 0.957588 + j 0.8422 [\Omega]$

12

07 : Z_{M13} , $Z_{M31} \Rightarrow Z_{ALL}$ [F-22]If $Z_{ALL} = R_{ALL} + jX_{ALL}$, $R_{M13} = 0.405268$ $X_{M13} = 0.29688$ $R_{M31} = 0.957588$ $X_{M31} = 0.8422$ $Z_{ALL} = 0.285511 + j 0.220409 [\Omega]$

17

08 : Z_{ALL} , $Z_{02} \Rightarrow Z_{002}$ [F-24] $E_s[V] = 220$

SC[KVA]= 75

The completion

 $Z_{02} : Z = E^2 / [KVar] = 220^2 / (75 \cdot 10^3) = 0.645333 [\Omega]$, $1/X_{02} = \sqrt{3} \cdot 0.645 \rightarrow X_{02} = 0.894654 [\Omega]$ If $Z_{002} = R_{002} + jX_{002}$, $R_{ALL} = 0.285511$ $X_{ALL} = 0.220409$ $X_{02} = 0.894654$ $Z_{002} = 0.402269 + j 0.146554 [\Omega]$

23

09 : Z_{002} , $Z_{01} \Rightarrow Z_{001}$ [F-11]

TR[KVA]= 300

IR[% R]= 1.4100

IR[% X]= 3.26

 $E_s[V] = 220$

The completion

 $Z_{01} : Z = E^2 / [KVar] = 220^2 / (300 \cdot 10^3) = 0.161333 [\Omega]$ $R_{01} = \sqrt{3} \cdot 0.1613 \cdot (1.41/100) = 0.00394 [\Omega]$, $X_{01} = \sqrt{3} \cdot 0.1613 \cdot (3.26/100) = 0.00911 [\Omega]$ $R_{002} = 0.402269$ $X_{002} = 0.146554$ $R_{01} = 0.00394$ $X_{01} = 0.00911$ $Z_{001} = 0.406209 + j 0.155664 [\Omega]$

30

10 : Z_{15} , $Z_{16} \Rightarrow \cos \phi$ [F-26] $R_{15} = 0.377241$ $X_{15} = 0.502988$ $X_{16} = 0.596436$ $Z_{M21} = 0.697786 + j 0.494265 [\Omega]$ $\cos \phi = 0.81602$

35

11 : $I_{01} = E_s / Z_{001}$ (Transformer current) $Z_{001} = 0.406209 + j 0.155664 [\Omega]$ $E_s[V] = 220$

The completion

 $I_{01} = 505.7306 [A]$

40

12 : $E_R = I_{01} \times Z_{002}$ (Power distribution side voltage) $Z_{002} = 0.402269 + j 0.146554 [\Omega]$ $I_{01}[A] = 505.7306 [A]$ $E_R = 216.5205 [V]$

44

45



1

$$13 : I_{ALL} = E_R / Z_{ALL} \text{ (All load current)}$$

$$Z_{ALL} = 0.285511 + j \ 0.220409 \ [\Omega] \quad E_R = 216.5205 \ [V]$$

$$I_{ALL} = 600.297 \ [A]$$

5

6

$$14 : I_{21} = E_R / Z_{M31} \text{ (Load current : M-3)}$$

$$Z_{M31} = 0.957588 + j \ 0.8422 \ [\Omega] \quad E_R = 216.5205 \ [V]$$

$$I_{21} = 169.786 \ [A]$$

10

$$15 : E_{22} = I_{21} \times Z_{22} \text{ (Primary board side terminal voltage : M-3)}$$

$$Z_{22} = 0.943102 + j \ 0.831737 \ [\Omega] \quad I_{21} = 169.786 \ [A]$$

$$E_{22} = 213.5006 \ [V]$$

14

15

$$16 : I_{11} = E_R / Z_{M13} \text{ (Load current : M-1, -2)}$$

$$Z_{M13} = 0.405268 + j \ 0.29688 \ [\Omega] \quad E_R = 216.5205 \ [V]$$

$$I_{11} = 430.9948 \ [A]$$

19

$$17 : E_B = I_{11} \times Z_{M12} \text{ (Branch part voltage)}$$

$$Z_{M12} = 0.394243 + j \ 0.286342 \ [\Omega] \quad I_{11} = 430.9948 \ [A]$$

$$E_B = 210.0053 \ [V]$$

23

$$18 : I_{12} = E_B / Z_{M11} \text{ (Load current : M-1)}$$

$$Z_{M11} = 0.899667 + j \ 0.673403 \ [\Omega] \quad E_B = 210.0053 \ [V]$$

$$I_{12} = 186.8747 \ [A]$$

27

$$19 : E_{14} = I_{12} \times Z_{14} \text{ (Primary board side terminal voltage : M-1)}$$

$$Z_{14} = 0.8942 + j \ 0.67065 \ [\Omega] \quad I_{12} = 186.8747 \ [A]$$

$$E_{14} = 208.8792 \ [V]$$

31

32

$$20 : I_{13} = E_B / Z_{M22} \text{ (Load current : M-2)}$$

$$Z_{M22} = 0.701461 + j \ 0.497778 \ [\Omega] \quad E_B = 210.0053 \ [V]$$

$$I_{13} = 244.1542 \ [A]$$

36

$$21 : E_{15} = I_{13} \times Z_{M21} \text{ (Primary board side terminal voltage : M-2)}$$

$$Z_{M21} = 0.697786 + j \ 0.494265 \ [\Omega] \quad I_{13} = 244.1542 \ [A]$$

$$E_{15} = 208.7773 \ [V]$$

40



41

The above and the manual calculation result of 1 to 21 are the following page. Please check that it is in agreement with each value of a 4-1 VD4 calculation sheet. The value of VD4 data sheet was used for each data required for manual calculation.

45

Trunk number	Application section	Electric system	Distribution side apparatus			Load side apparatus										Selection-1 (Branch trunk)			Selection-2 (Trunk)			Transmission	Reception			Distribution side		Remarks							
		Sec. voltage Es[V] φ W V	Power transformer		SCs Capacity [Kvar]	Load equipment capacity										Cable name	Construct	Cable name	Construct	Voltage Er [V]	Voltage El [V]	Current Il [A]	Breaker												
			Form	Number % Z		Load classification	Output [KW]	Efficiency η	Power factor cos φ	Input [KVA]	Demand factor Df	Load current [A]	ZL [Ω]	Rc [Ω]	Zc1 (Trunk)									Zc2 (Branch trunk)	Branch part [V]	Zr1 (Lr+C1)	-AF		-AT						
																														Frequency [Hz]	Capacity/Rated current	All load [A]	El/Er [%]	Current Ic [A] (Total)	Name
F-01	Outdoor form CB (TR-1) power switchboard → M-1 power board	3 φ 3 W 220 V	oil cooled type	1	75.0	M-1	60.0	1.000	0.800	75.00	1.00	196.8	1.1178	0.8000	600V CV-T	Cabletra y	600V CV-T	Exposure piping	216.52 [V]	208.88 [V]	186.87 [A]	MCCB-3P 600 500	Load factor of TR-1 64.23 % TR-1 voltage rate of change 3.47 [V] 1.58%												
		60.0 [Hz]	300.0 [KVA]							0.8942		200.0 [2] 120.0[m]	100.0 [1] 15.0[m]				216.52 [V]	94.9451 [%]	600.30 [A]																
		50.0 [°C]	787.3 [A]							0.6707		11.0244 + j 10.5378 [mΩ]	5.4667 + j 2.7529 [mΩ]				505.73 [A]	5.0549 [%]	600.30 [A]																
	F-01 trunk branch P-Box → M-2 power board					M-2	80.0	1.000	0.600	133.33	1.00	349.9	0.6287	0.8160			600V CV-T	Exposure piping		208.78 [V]	244.15 [A]														
		Prod. power								0.3772		200.0 [1] 20.0[m]					94.8988 [%]	244.15 [A]																	
										0.5030		3.6748 + j 3.5126 [mΩ]					210.01 [V]	0.6978 + j 0.4943 [Ω]																	
		50.0 [°C]																																	
F-02	Outdoor form CB (TR-1) power switchboard → M-3 power board					M-3	50.0	1.000	0.750	66.67	1.00	175.0	1.2575	0.7500	600V CV-T	Cabletra y			216.52 [V]	213.50 [V]	169.79 [A]	MCCB-3P 225 225													
		Prod. power								0.9431		150.0 [1] 60.0[m]					97.0457 [%]																		
										0.8317		14.4866 + j 10.4630 [mΩ]					2.9543 [%]																		
		50.0 [°C]																																	
F-01	Outdoor form CB (TR-1) power switchboard → M-1 power board	3 φ 3 W 220 V	oil cooled type	1	100.0	M-1	60.0	1.000	0.800	75.00	1.00	196.8	1.1178	0.8000	600V CV-T	Cabletra y	600V CV-T	Exposure piping	217.10 [V]	209.43 [V]	187.37 [A]	MCCB-3P 600 500	Load factor of TR-1 62.07 % TR-1 voltage rate of change 2.9 [V] 1.31%												
		60.0 [Hz]	300.0 [KVA]							0.8942		200.0 [2] 120.0[m]	100.0 [1] 15.0[m]				217.10 [V]	95.1977 [%]	601.89 [A]																
		50.0 [°C]	787.3 [A]							0.6707		11.0244 + j 10.5378 [mΩ]	5.4667 + j 2.7529 [mΩ]				488.71 [A]	4.8023 [%]	601.89 [A]																
	F-01 trunk branch P-Box → M-2 power board					M-2	80.0	1.000	0.600	133.33	1.00	349.9	0.6287	0.8160			600V CV-T	Exposure piping		209.33 [V]	244.80 [A]														
		Prod. power								0.3772		200.0 [1] 20.0[m]					95.1513 [%]	244.80 [A]																	
										0.5030		3.6748 + j 3.5126 [mΩ]					4.8487 [%]																		
		50.0 [°C]																																	
F-02	Outdoor form CB (TR-1) power switchboard → M-3 power board					M-3	50.0	1.000	0.750	66.67	1.00	175.0	1.2575	0.7500	600V CV-T	Cabletra y			217.10 [V]	214.07 [V]	170.24 [A]	MCCB-3P 225 225													
		Prod. power								0.9431		150.0 [1] 60.0[m]					97.3039 [%]																		
										0.8317		14.4866 + j 10.4630 [mΩ]					2.6961 [%]																		
		50.0 [°C]																																	
F-01	Outdoor form CB (TR-1) power switchboard → M-1 power board	3 φ 3 W 220 V	oil cooled type	1	75.0	M-1	60.0	1.000	0.800	75.00	1.00	196.8	1.1178	0.8000	600V CV-T	Cabletra y	600V CV-T	Exposure piping	145.32 [V]	140.19 [V]	125.43 [A]	MCCB-3P 600 500	Load factor of TR-1 1056.48 % TR-1 voltage rate of change 74.67 [V] 33.94%												
		60.0 [Hz]	300.0 [KVA]							0.8942		200.0 [2] 120.0[m]	100.0 [1] 15.0[m]				145.32 [V]	63.7249 [%]	8393.15 [A]																
		50.0 [°C]	787.3 [A]							0.6707		11.0244 + j 10.5378 [mΩ]	5.4667 + j 2.7529 [mΩ]				8317.63 [A]	36.2751 [%]	8393.15 [A]																
	F-01 trunk branch P-Box → M-2 power board					M-2	80.0	1.000	0.600	133.33	1.00	349.9	0.6287	0.8160			600V CV-T	Exposure piping		140.13 [V]	163.87 [A]														
		Prod. power								0.3772		200.0 [1] 20.0[m]					63.6938 [%]	163.87 [A]																	
										0.5030		3.6748 + j 3.5126 [mΩ]					36.3062 [%]																		
		50.0 [°C]																																	
F-02	Outdoor form CB (TR-1) power switchboard → M-3 power board					M-3	1000000	1.000	0.750	1333333.33	1.00	3498092.5	0.0001	0.7500	600V CV-T	Cabletra y			145.32 [V]	.51 [V]	8103.88 [A]	MCCB-3P 225 225	Short current of M-3 8.1038 [KA]												
		Prod. power								0.0000		150.0 [1] 60.0[m]					0.2316 [%]																		
										0.0000		14.4866 + j 10.4630 [mΩ]					99.7684 [%]																		
		50.0 [°C]																																	

Circuit diagram

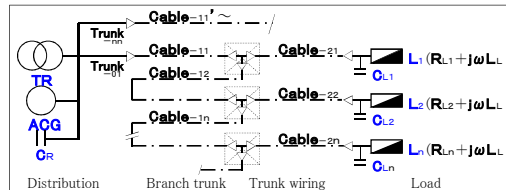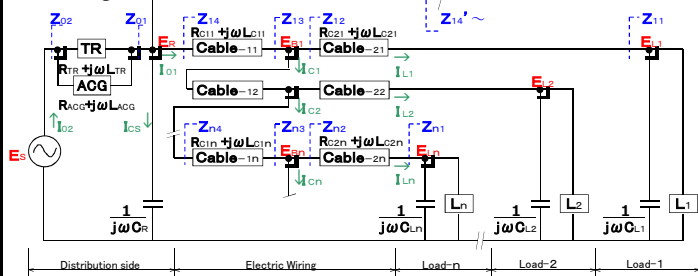

Distribution side $E_r = I_{02} \cdot Z_{01}$ Transformer current $I_{02} = E_s / Z_{02}$ [A]
All load current $I_{01} = E_r / Z_{14}$ [A]

Load side voltage $E_L = (Z_{01} \cdot Z_{13} \cdot Z_{11}) \cdot E_s / (Z_{02} \cdot Z_{14} \cdot Z_{12})$ [V]
Load side current $I_{L1} = (Z_{01} \cdot Z_{13}) \cdot E_s / (Z_{02} \cdot Z_{14} \cdot Z_{12})$ [A]

This calculation is based on the Ohm method.

Memo.

Project Name	4-1 VD4 Calculation sheet	Exchange circuit analysis calculation-VD4 Electro Systems Engineering Service	Approved K. Sakai	Checked	Terminal voltage -01
--------------	---------------------------	--	----------------------	---------	-------------------------

[illegible]

[illegible]

Notes-1) Let the rate of load be the average value of the induction motor of the right above grade to Calculation axis power [KW] × (1 + margin [%]).
Notes-2) The efficiency and powerfactor to the rate of load of an induction motor are computed by straight line proportionality calculation from a value 50 or 75,100%.

Margin of motor selection[%]→ **10**

50Hz-200V		EFF(%)	PF(%)
Output KW	Load factor		
0.15			
0.20	79.55	71.95	65.02
0.40	68.18	75.98	65.83
0.75	69.70	80.49	65.41
1.50	68.18	82.37	63.59
2.20	76.45	86.67	72.20
3.70	72.48	87.04	72.49
5.50	76.03	89.28	75.88
7.50	78.79	89.42	78.39
11.00	76.45	91.88	76.46
15.00	78.79	92.27	78.38
18.50	82.31	92.80	78.13
22.00	83.68	93.06	81.60
30.00	78.79	92.92	80.01
37.00	82.31	94.00	85.59
45.00	82.83	92.84	82.28
55.00	82.64	94.01	80.87

FEE,PF of Induction motor (50Hz-200V)					
at 50% Load		at 75% Load		at 100% Load	
EFF(%)	PF(%)	EFF(%)	PF(%)	EFF(%)	PF(%)
68.1	50.8	71.9	63.4	72.2	72.3
74.6	57.1	76.5	69.1	76.0	77.8
78.6	55.4	81.0	68.1	80.5	76.0
80.7	54.5	83.0	67.0	83.1	75.1
85.4	59.6	86.7	71.8	86.1	78.7
86.5	61.7	87.1	73.7	86.3	80.4
88.3	63.4	89.3	75.6	88.9	82.4
88.8	65.3	89.5	77.5	89.0	83.4
91.3	64.7	91.9	76.1	91.5	82.3
91.6	66.3	92.3	77.5	92.1	83.3
91.9	64.5	92.8	76.4	92.8	82.3
92.7	69.1	93.2	80.0	92.8	84.6
92.7	68.1	93.0	79.3	92.5	84.0
93.9	77.1	94.2	84.8	93.5	87.5
92.4	70.7	92.9	81.0	92.7	85.1
93.9	68.4	94.1	79.0	93.8	85.1

60Hz-220V		EFF(%)	PF(%)
Output KW	Load factor		
0.15			
0.20	79.55	75.09	64.63
0.40	68.18	78.60	66.51
0.75	69.70	83.21	66.27
1.50	68.18	85.18	57.21
2.20	76.45	88.59	73.18
3.70	72.48	88.41	73.02
5.50	76.03	90.20	77.63
7.50	78.79	90.45	79.37
11.00	76.45	92.59	77.73
15.00	78.79	92.68	80.11
18.50	82.31	93.23	80.08
22.00	83.68	93.53	82.65
30.00	78.79	93.28	82.24
37.00	82.31	93.65	86.52
45.00	82.83	93.71	84.86
55.00	82.64	94.54	83.58

FEE,PF of Induction motor (60Hz-220V)					
at 50% Load		at 75% Load		at 100% Load	
EFF(%)	PF(%)	EFF(%)	PF(%)	EFF(%)	PF(%)
71.1	51.2	75.0	63.1	75.5	71.5
77.0	58.0	79.2	69.7	78.8	77.2
81.4	56.5	83.7	68.9	83.3	76.2
83.8	55.1	85.7	58.0	85.8	75.9
87.4	61.0	88.6	72.8	88.5	79.4
87.6	62.5	88.5	74.2	88.1	80.6
89.0	66.1	90.2	77.4	90.1	83.0
89.6	67.5	90.5	78.6	90.2	83.7
92.0	67.4	92.6	77.4	92.4	83.1
91.8	68.4	92.7	79.4	92.6	84.1
92.3	67.7	93.2	78.5	93.3	83.9
92.9	71.8	93.6	81.3	93.4	85.2
92.6	72.1	93.3	81.6	93.2	85.8
93.1	79.1	93.8	85.7	93.3	88.5
93.2	75.5	93.8	83.8	93.5	87.2
94.1	73.0	94.6	82.2	94.4	86.7

5-3 DATA sheet



6 Exchange circuit analysis by VD4

Following, The contents of description of 6-1 and 6-2 can be performed if each input value is corrected with VD4 calculation sheet. Please correct an item to change and realize an output value and calculation speed.

6-1 Short-circuit current calculation

If 50 [KW] of the load side apparatus output KW (cell number [P58]) of a 4-1 VD4 calculation sheet is changed into 1000000[KW], The short-circuit current 8.1038[KA] (symmetrical value) by the side of primary [of an on-site board (M-3)] is called for. Moreover, if Output KW is made into 100000[KW], a short-circuit current will be set to 7.9375[KA]. The contact resistance by the short circuit accident at this time becomes $0.0005 + j0.0004[\Omega]$. Next, if the span of an F-02 trunk cable is made into 0 [m] in order to ask for the short-circuit current by the side of transformer secondary (symmetrical value), 22.0374 [KA] will be outputted to a remarks column. Cell number : refer to Z60 and AL59

6-2 About a power factor improvement

If 75 [Kvar] of the power distribution side apparatus SC_R (cell number [N18]) of a 4-1 VD4 calculation sheet is made into "DEL", the following value will change.

1) All load current [A] :	600. 30 → 595. 55
2) Power distribution side voltage [V] :	216. 52 → 214. 81
3) Transformer current[A] :	505. 73 → 595. 55
4) Load factor of transformer [%] :	64. 23 → 75. 67
5) Transformer voltage rate of change[%] :	1. 58 (3. 47 [V]) → 2. 35 (5. 19 [V])
6) M-1 Terminal voltage[V] :	208. 88 → 207. 23
M-2 Terminal voltage[V] :	208. 78 → 207. 13
M-3 Terminal voltage[V] :	213. 50 → 211. 81
Load current[A] :	186. 87 → 185. 40
Load current[A] :	244. 15 → 242. 22
Load current[A] :	169. 79 → 168. 44

Next, if this SC_R is made into 100 [Kvar], the above-mentioned value will change conversely.
Column number : refer from 34 to 45

6-3 About a series reactor

In VD4, the input of an in-series reactor is unnecessary. When the in-series reactor is installed, since the capacity equivalent to a reactor is expected, to the power capacitor, this calculation is unnecessary.

6-4 Reliability of Load list

A Load list is created in order to grasp the special feature of load. Therefore, the track reactance drop by wiring is not taken into consideration. Although load side apparatus [load current] of VD4 disregards the voltage rate of change of a transformer and is displayed as a reference value over rated voltage, an actual load current value turns into a value smaller than this. It is a value (64.23% → 67.58%) with the more larger actually rate of transformer of a Load list also from this.

7 The plan of electric equipment

7-1 Master plan

The master plan document and examination document which are hung up over the next can be drawn up by **VD4** and **Load list**.

- 1) The number and rated capacity of the power transformer can be assumed by **Load list**.
- 2) Determination of a incoming system and incoming voltage, and assumption of an electric system.
- 3) Assumption of a power factor improvement system.
- 4) Assumption of the number of circuits of a trunk, and trunk size.

7-2 Enforcement plan

The data base for a Enforcement plan which are hung up over the next can be drawn up by **VD4** and **Load list**.

- 1) Road list can determine the number and rated capacity of the power transformer.
- 2) The determination of an electric system. Assumption of primary terminal voltage and load current of on-site board.
- 3) Determination of a power factor improvement system, and assumption of improvement power factor.
- 4) Determination of the number of circuits of a trunk, and trunk size. Assumption of a trunk margin.

8 Maintenance management of electric equipment

8-1 Various imitation construction

VD4 can perform the next imitation construction.

- 1) Tap adjustment of the power transformer accompanying incoming voltage change.
- 2) Change construction of an electric system.
- 3) Establishment, extension, withdrawal, or replacement construction of a power transformer and a power capacitor.
- 4) Route change construction or exchange construction of a trunk cable accompanying load capacity change.
- 5) The short circuit examination in a required part. (symmetrical value)

8-2 Various diagnostic tests

VD4 can perform the next diagnostic test.

- 1) The transformer capacity check and wiring capacity check accompanying load change.
- 2) The check of margin of a trunk cable. The countermeasure check accompanying the increase in load capacity
- 3) The check of the terminal voltage by reexamination of circumference temperature.
- 4) The check of power capacitor capacity and the minimum power factor.
- 5) Guess the route by calculating the span of the old trunk cable which is unknown. etc.

8-3 Karte [Data base] registration

You have to cope with quickly future extension-and-alteration construction, renewal construction of apparatus, etc. by database-izing of the present electric equipment. It is important in order that this may aim at safety of electric equipment, and efficient employment [sick prevention]. Furthermore, if the **Load list** which is the foundation of each load data of **VD4** is also data-base-ized collectively, it is much more thoroughgoing.